 




# University of Tehran Electrical and Computer Engineering Department Computer Architecture Computer Assignment #4 MIPS Pipeline

| Name       | Danial Saeedi             |  |  |  |
|------------|---------------------------|--|--|--|
|            | Mohammad Ghare Hasanloo   |  |  |  |
| Student No | 810198571                 |  |  |  |
|            | 810198461                 |  |  |  |
| Date       | Tuesday - 2022 04 January |  |  |  |

# 1. Datapath



### 2. Control Unit

|      | ALUOp | MemtoReg | Reg_Write | Mem_Read | Reg_Write | Branch | ALUsrc | ld | regDst | writeDst | Mem_Write | Jump |
|------|-------|----------|-----------|----------|-----------|--------|--------|----|--------|----------|-----------|------|
| add  | 101   | 0        | 1         | 0        | 0         | 0      | 1      | 0  | 0      | 000      | 0         | 00   |
| sub  | 101   | 0        | 1         | 0        | 0         | 0      | 1      | 0  | 0      | 000      | 0         | 00   |
| and  | 101   | 0        | 1         | 0        | 0         | 0      | 1      | 0  | 0      | 000      | 0         | 00   |
| or   | 101   | 0        | 1         | 0        | 0         | 0      | 1      | 0  | 0      | 000      | 0         | 00   |
| slt  | 101   | 0        | 1         | 0        | 0         | 0      | 1      | 0  | 0      | 000      | 0         | 00   |
| addi | 000   | 1        | 0         | 0        | 0         | 0      | 1      | 0  | 0      | 000      | 0         | 00   |
| slti | 011   | 1        | 0         | 0        | 0         | 0      | 1      | 0  | 0      | 000      | 0         | 00   |
| lw   | 000   | 0        | 1         | 1        | 0         | 0      | 1      | 0  | 0      | 100      | 0         | 00   |
| sw   | 000   | 0        | 0         | 0        | 0         | 0      | 1      | 0  | 0      | 000      | 1         | 00   |
| beq  | 001   | 0        | 0         | 0        | 0         | 1      | 0      | 0  | 0      | 000      | 0         | 00   |
| j    | 0     | 0        | 0         | 0        | 0         | 0      | 0      | 0  | 0      | 000      | 0         | 01   |
| jr   | 0     | 0        | 0         | 0        | 0         | 0      | 0      | 0  | 0      | 000      | 0         | 10   |
| jal  | 0     | 0        | 1         | 0        | 0         | 0      | 0      | 0  | 1      | 001      | 0         | 01   |

# 3. ALU Truth Table & Controller

| ALUop | ALUoperation | func |
|-------|--------------|------|
| 000   | 0000         | x    |
| 001   | 0111         | ×    |
| 010   | 1000         | x    |
| 011   | 0110         | ×    |
| 100   | 0010         | ×    |
| 101   | 0000         | add  |
| 101   | 0001         | sub  |
| 101   | 0011         | and  |
| 101   | 0100         | or   |
| 101   | 0101         | xor  |
| 101   | 0110         | slt  |

| ALU_Sel | Output           |
|---------|------------------|
| 0000    | In1 + In2        |
| 0001    | ln1 - ln2        |
| 0011    | In1 & In2        |
| 0100    | In1   In2        |
| 0101    | In1 ^ In2        |
| 0110    | slt              |
| 0111    | Branch Equal     |
| 1000    | Branch Not Equal |

# **Testbench**

